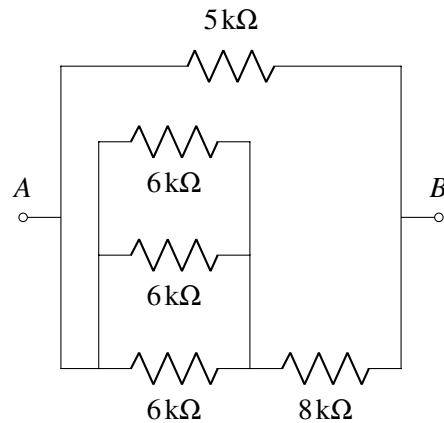


EECS 16A Designing Information Devices and Systems I

Spring 2020 Discussion 7B

1. Series and Parallel Combinations

For the resistor network shown below, find an equivalent resistance between the terminals A and B using the resistor combination rules for series and parallel resistors.





Answer:

$$5 \text{ k}\Omega \parallel ((6 \text{ k}\Omega \parallel 6 \text{ k}\Omega \parallel 6 \text{ k}\Omega) + 8 \text{ k}\Omega) = 5 \text{ k}\Omega \parallel (2 \text{ k}\Omega + 8 \text{ k}\Omega) = 5 \text{ k}\Omega \parallel 10 \text{ k}\Omega = 3.33 \text{ k}\Omega$$


2. Series And Parallel Capacitors

Derive C_{eq} for the following circuits.

(a) (b)

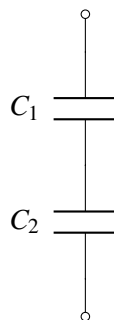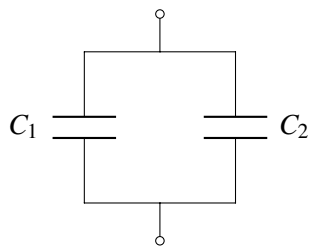

(c)

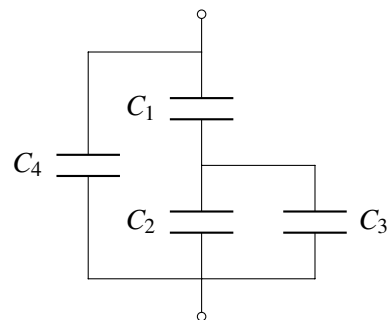


Answer:

(a)

$$C_{eq} = C_1 + C_2$$

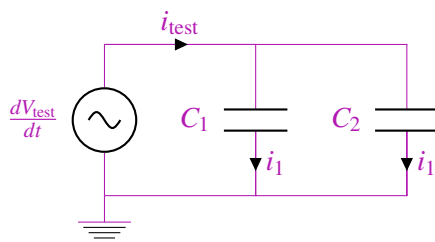Notice these capacitors are in parallel. We can derive their equivalent capacitance by connecting them to a voltage source with a constant derivative, as shown by the circuit below:




Since both capacitors have the same voltage across them:

$$\begin{aligned}\frac{dV_{C_1}}{dt} &= \frac{dV_{C_2}}{dt} = \frac{dV_{\text{test}}}{dt} \\ i_1 &= C_1 \frac{dV_{\text{test}}}{dt} \\ i_2 &= C_2 \frac{dV_{\text{test}}}{dt} \\ i_t &= i_1 + i_2 = (C_1 + C_2) \frac{dV_{\text{test}}}{dt}\end{aligned}$$

Since we know $i_{\text{test}} = C_{\text{eq}} \frac{dV_{\text{out}}}{dt}$,

$$C_{\text{eq}} = C_1 + C_2$$

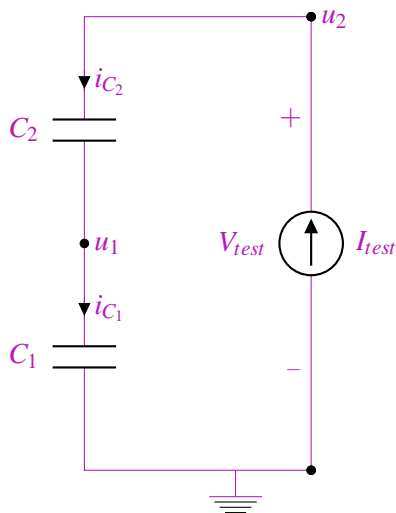- (b) In order to find the equivalence capacitance of the circuit, we plug in a test current source, and measure the rate of change of voltage across it.



From KCL, we know that all of the currents are equal.

$$i_{C_1} = i_{C_2} = I_{\text{test}}$$

For each capacitor, we plug in our $I - \frac{dV}{dt}$ relationship:

$$i_{C_1} = I_{\text{test}} = C_1 \frac{du_1}{dt}$$

$$i_{C_2} = I_{test} = C_2 \frac{d(u_2 - u_1)}{dt} = C_2 \left(\frac{du_2}{dt} - \frac{du_1}{dt} \right)$$

Next, we eliminate u_1 from the equations above and rearrange.

$$\frac{du_1}{dt} = \frac{I_{test}}{C_1} \Rightarrow I_{test} = C_2 \frac{du_2}{dt} - \frac{C_2}{C_1} I_{test}$$

$$I_{test} = \frac{C_2}{1 + \frac{C_2}{C_1}} \frac{du_2}{dt}$$

Finally, we plug in that $u_2 = V_{test}$ and solve for the equivalent capacitance with $C_{eq} = I_{test} / \frac{dV_{test}}{dt}$

$$I_{test} = \frac{C_2}{1 + \frac{C_2}{C_1}} \frac{dV_{test}}{dt}$$

$$\Rightarrow C_{eq} = \frac{C_2}{1 + \frac{C_2}{C_1}} = \frac{C_1 C_2}{C_1 + C_2}$$


Note that this is the same as saying $C_{eq} = C_1 \parallel C_2$. Remember that the \parallel operator is mathematical notation; in this case, the capacitors are actually in series, but *mathematically* their equivalent circuit is found via the “parallel resistor” operation.

- (c) Given that we know what the relationship for capacitors in series and parallel are from the last two parts, we can just simply the capacitors step by step:

$$C_{eq} = (C_4 + (C_1 \parallel (C_2 + C_3))) = \frac{C_4(C_1 + C_2 + C_3) + C_1(C_2 + C_3)}{C_1 + C_2 + C_3}$$

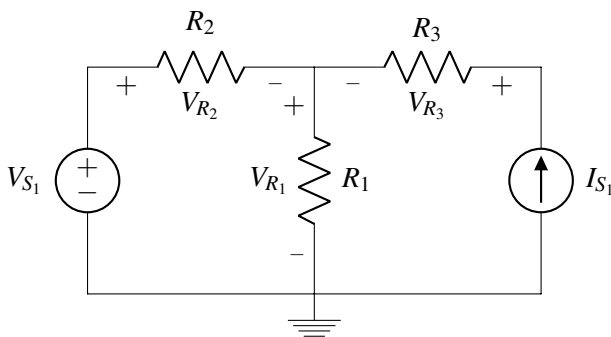3. Superposition

For the following circuit, use the superposition theorem to solve for the voltages across the resistors.



Answer: Turning on only V_{S_1} , we have the following voltages across the resistors:

$$V_{R_1} = \frac{R_1}{R_1 + R_2} V_{S_1}$$

$$V_{R_2} = \frac{R_2}{R_1 + R_2} V_{S_1}$$

$$V_{R_3} = 0$$

Then turning only I_{S_1} , we have the following voltages:

$$V_{R_1} = \frac{R_1 R_2}{R_1 + R_2} I_{S_1}$$

$$V_{R_2} = -\frac{R_1 R_2}{R_1 + R_2} I_{S_1}$$

$$V_{R_3} = I_{S_1} R_3$$

Using superposition we can sum up the contributions from both V_{S_1} and I_{S_1} to get:

$$V_{R_1} = \frac{R_1}{R_1 + R_2} V_{S_1} + \frac{R_1 R_2}{R_1 + R_2} I_{S_1}$$


$$V_{R_2} = V_{S_1} - V_{R_1} = \frac{R_2}{R_1 + R_2} V_{S_1} - \frac{R_1 R_2}{R_1 + R_2} I_{S_1}$$

$$V_{R_3} = I_{S_1} R_3$$

4. Current Sources And Capacitors

For the circuits given below, give an expression for $v_{\text{out}}(t)$ in terms of I_s , C_1 , C_2 , and t . Assume that all capacitors are initially uncharged, i.e. the initial voltage across each capacitor is 0V.

(a)

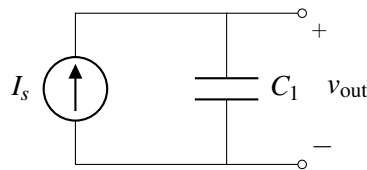


Answer:

$$I_s = C_1 \frac{dv_{\text{out}}(t)}{dt}$$

$$v_{\text{out}}(t) = \int \frac{I_s}{C_1} dt = \frac{I_s t}{C_1} + v_{\text{out}}(0)$$

Since the capacitor is initially uncharged, $v_{\text{out}}(0) = 0$, so $v_{\text{out}}(t) = \frac{I_s t}{C_1}$.

(b)

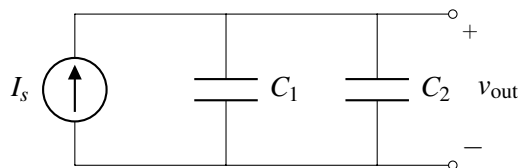

Answer:

We can combine the two capacitors into an equivalent capacitor with capacitance $C_1 + C_2$. Again, $v_{\text{out}}(0) = 0$ because all capacitors are initially uncharged.

$$I_s = (C_1 + C_2) \frac{dv_{\text{out}}(t)}{dt}$$

$$v_{\text{out}}(t) = \frac{I_s t}{C_1 + C_2} + v_{\text{out}}(0) = \frac{I_s t}{C_1 + C_2}$$