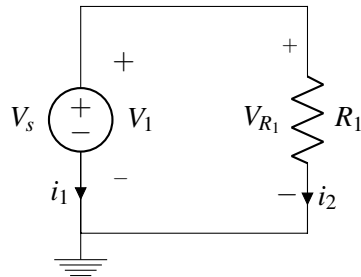
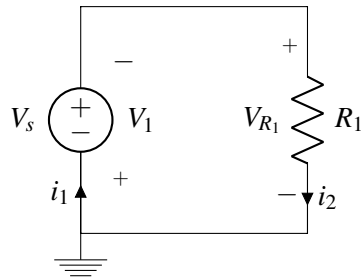

EECS 16A Designing Information Devices and Systems I Discussion 7A
 Spring 2020

1. Passive Sign Convention and Power

- (a) Suppose we have the following circuit and label the currents as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let $V_s = 5\text{ V}$ and let $R_1 = 5\ \Omega$.




- (b) Suppose we change the label of the currents in the circuit to be as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let $V_s = 5\text{ V}$ and let $R_1 = 5\ \Omega$.




2. Circuit Analysis

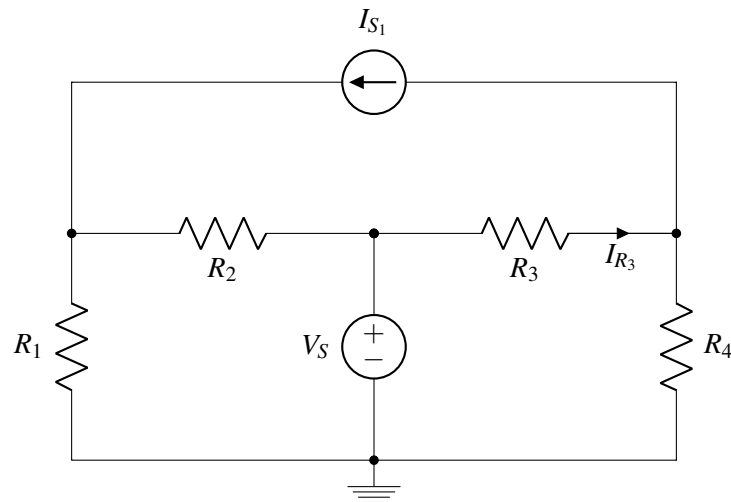- (a) Use nodal analysis to solve for all node voltages.
 (b) Find current I_{R_3} flowing through resistor R_3 .



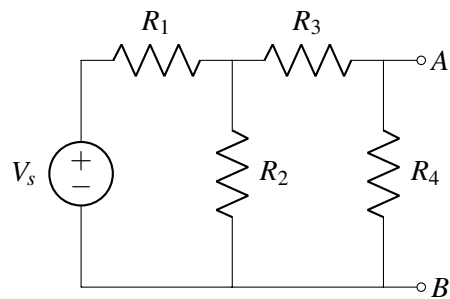3. KVL and KCL

For the circuit shown below, $V_s = 5\text{ V}$, $R_1 = R_2 = 4\text{ k}\Omega$, and $R_3 = R_4 = 2\text{ k}\Omega$.



- For the circuit above, write KVL equations for each loop and KCL equations for each node.
- Solve for the voltage between A and B using resistor combination rules and divider rules.