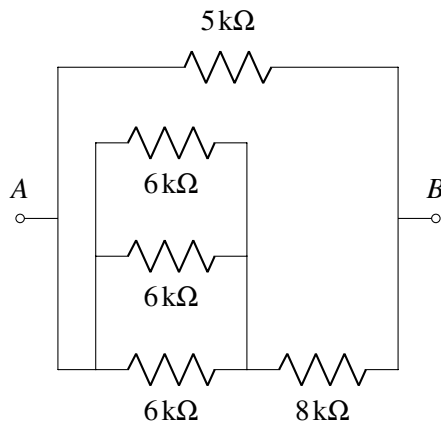

EECS 16A Designing Information Devices and Systems I Discussion 7B
 Spring 2020


1. Series and Parallel Combinations

For the resistor network shown below, find an equivalent resistance between the terminals *A* and *B* using the resistor combination rules for series and parallel resistors.



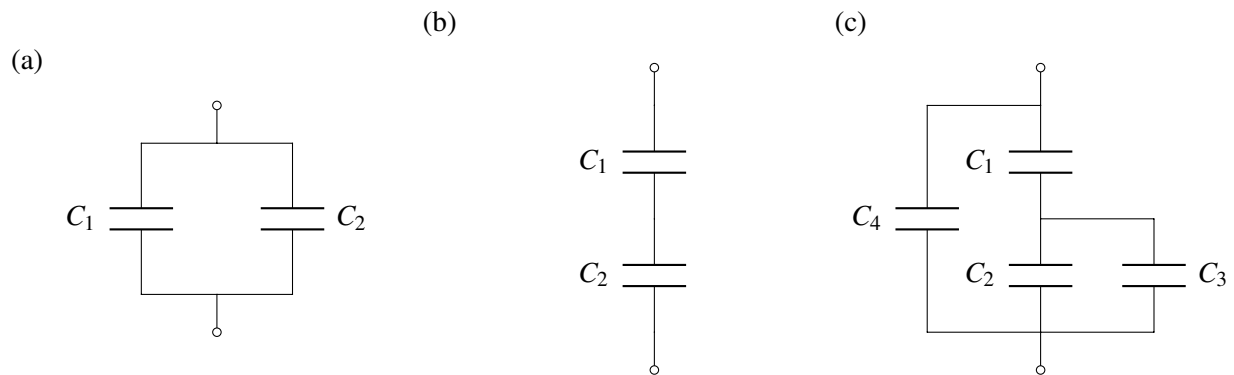2. Series And Parallel Capacitors

Derive C_{eq} for the following circuits.




3. Superposition


For the following circuits:

- i. Use the superposition theorem to solve for the voltages across the resistors.
- ii. For parts (a) and (b) only, find the power dissipated/generated by all components. Is power conserved?


(a)

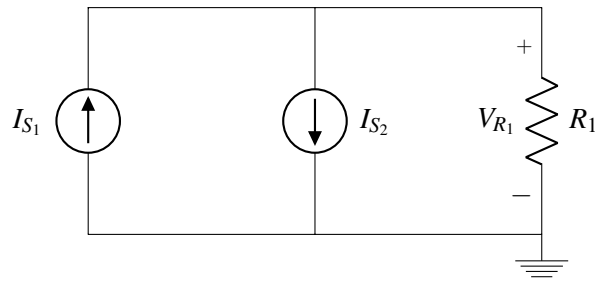

(b)

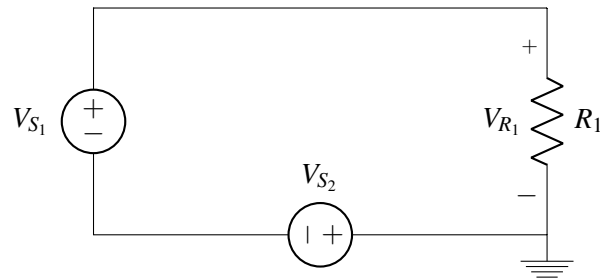


(c)

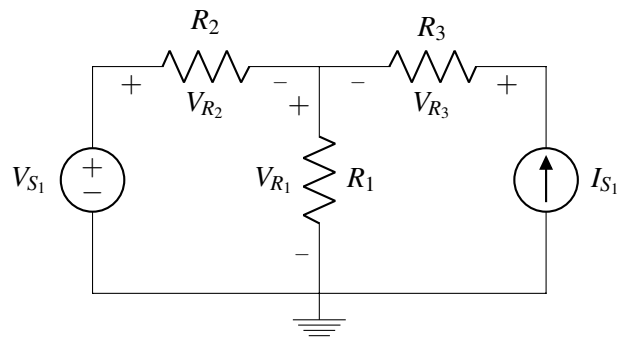

4. Current Sources And Capacitors

For the circuits given below, give an expression for $v_{out}(t)$ in terms of I_s , C_1 , C_2 , and t . Assume that all capacitors are initially uncharged, i.e. the initial voltage across each capacitor is 0V.

(a)

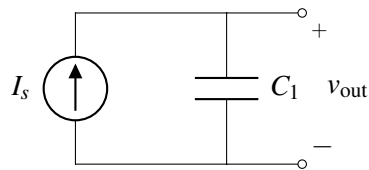

(b)

